

NPN Transistor


NPN Transistors are three-terminal, three-layer devices that can function as either amplifiers or electronic switches

In the previous tutorial we saw that the standard **Bipolar Transistor** or BJT, comes in two basic forms. An **NPN** (Negative-Positive-Negative) type and a **PNP** (Positive-Negative-Positive) type.

The most commonly used transistor configuration is the **NPN Transistor**. We also learnt that the junctions of the bipolar transistor can be biased in one of three different ways – **Common Base**, **Common Emitter** and **Common Collector**.


In this tutorial about bipolar transistors we will look more closely at the “Common Emitter” configuration using the **Bipolar NPN Transistor** with an example of the construction of a NPN transistor along with the transistors current flow characteristics is given below.

A Bipolar NPN Transistor Configuration

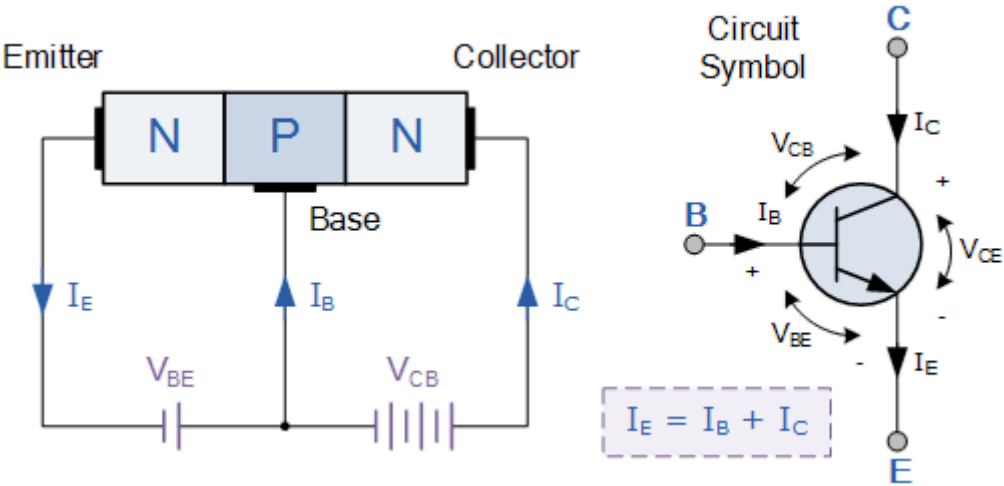

(Note: Arrow defines the emitter and conventional current flow, “out” for a Bipolar NPN Transistor.)

The construction and terminal voltages for a bipolar NPN transistor are shown above. The voltage between the Base and Emitter (V_{BE}), is positive at the Base and negative at the Emitter because for an NPN transistor, the Base terminal is always positive with respect to the Emitter. Also the Collector supply voltage is positive with respect to the Emitter (V_{CE}). So for a bipolar NPN transistor to conduct the Collector is always more positive with respect to both the Base and the Emitter.

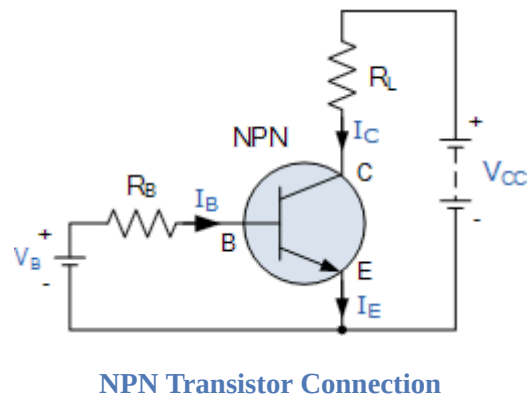

Then the voltage sources are connected to an NPN transistor as shown. The Collector is connected to the supply voltage V_{CC} via the load resistor, R_L which also acts to limit the maximum current flowing through the device. The Base supply voltage V_B is connected to the Base resistor R_B , which again is used to limit the maximum Base current.

So in a NPN Transistor it is the movement of negative current carriers (electrons) through the Base region that constitutes transistor action, since these mobile electrons provide the link between the Collector and Emitter circuits. This link between the input and output circuits is the main feature of transistor action because the transistors amplifying properties come from the consequent control which the Base exerts upon the Collector to Emitter current.

Then we can see that the transistor is a current operated device (Beta model) and that a large current (I_C) flows freely through the device between the collector and the emitter terminals when the transistor is switched “fully-ON”. However, this only happens when a small biasing current (I_b) is flowing into the base terminal of the transistor at the same time thus allowing the

Base to act as a sort of current control input.

The current in a bipolar NPN transistor is the ratio of these two currents (I_C/I_b), called the *DC Current Gain* of the device and is given the symbol of h_{fe} or nowadays Beta, (β).

The value of β can be large up to 200 for standard transistors, and it is this large ratio between I_C and I_b that makes the bipolar NPN transistor a useful amplifying device when used in its active region as I_b provides the input and I_C provides the output. Note that Beta has no units as it is a ratio.

Also, the current gain of the transistor from the Collector terminal to the Emitter terminal, I_C/I_e , is called Alpha, (α), and is a function of the transistor itself (electrons diffusing across the junction). As the emitter current I_e is the sum of a very small base current plus a very large collector current, the value of alpha (α), is very close to unity, and for a typical low-power signal transistor this value ranges from about 0.950 to 0.999

α and β Relationship in a NPN Transistor

$$\text{DC Current Gain} = \frac{\text{Output Current}}{\text{Input Current}} = \frac{I_C}{I_B}$$

$$I_E = I_B + I_C \text{ (KCL) } \text{ and } \frac{I_C}{I_E} = \alpha$$

$$\text{Thus: } I_B = I_E - I_C$$

$$I_B = I_E - \alpha I_E$$

$$I_B = I_E (1 - \alpha)$$

$$\therefore \beta = \frac{I_C}{I_B} = \frac{I_C}{I_E(1 - \alpha)} = \frac{\alpha}{1 - \alpha}$$

By combining the two parameters α and β we can produce two mathematical expressions that gives the relationship between the different currents flowing in the transistor.

$$\alpha = \frac{\beta}{\beta + 1} \text{ or } \alpha = \beta(1 - \alpha)$$

$$\beta = \frac{\alpha}{1 - \alpha} \text{ or } \beta = \alpha(1 + \beta)$$

$$\text{If } \alpha = 0.99 \quad \beta = \frac{0.99}{0.01} = 99$$

The values of Beta vary from about 20 for high current power transistors to well over 1000 for high frequency low power type bipolar transistors. The value of Beta for most standard NPN transistors can be found in the manufactures data sheets but generally range between 50 – 200.

The equation above for Beta can also be re-arranged to make Ic as the subject, and with a zero base current (Ib = 0) the resultant collector current Ic will also be zero, ($\beta \cdot 0$). Also when the base current is high the corresponding collector current will also be high resulting in the base current controlling the collector current. One of the most important properties of the **Bipolar Junction Transistor** is that a small base current can control a much larger collector current. Consider the following example.

NPN Transistor Example No1

A bipolar NPN transistor has a DC current gain, (Beta) value of 200. Calculate the base current Ib required to switch a resistive load of 4mA.

$$I_B = \frac{I_C}{\beta} = \frac{4 \times 10^{-3}}{200} = 20\mu\text{A}$$

Therefore, $\beta = 200$, $I_c = 4\text{mA}$ and $I_b = 20\mu\text{A}$.

One other point to remember about **Bipolar NPN Transistors**. The collector voltage, (Vc) must be greater and positive with respect to the emitter voltage, (Ve) to allow current to flow through the transistor between the collector-emitter junctions. Also, there is a voltage drop between the Base and the Emitter terminal of about 0.7V (one diode volt drop) for silicon devices as the input characteristics of an NPN Transistor are of a forward biased diode.

Then the base voltage, (Vbe) of a NPN transistor must be greater than this 0.7V otherwise the transistor will not conduct with the base current given as.

$$I_B = \frac{V_B - V_{BE}}{R_B}$$

Where: Ib is the base current, Vb is the base bias voltage, Vbe is the base-emitter volt drop (0.7v) and Rb is the base input resistor. Increasing Ib, Vbe slowly increases to 0.7V but Ic rises exponentially.

NPN Transistor Example No2

An NPN Transistor has a DC base bias voltage, Vb of 10v and an input base resistor, Rb of 100kΩ. What will be the value of the base current into the transistor.

$$I_B = \frac{V_B - V_{BE}}{R_B} = \frac{10 - 0.7}{100k\Omega} = 93\mu A$$

Therefore, $I_b = 93\mu A$.

The Common Emitter Configuration.

As well as being used as a semiconductor switch to turn load currents “ON” or “OFF” by controlling the Base signal to the transistor in either its saturation or cut-off regions, **Bipolar NPN Transistors** can also be used in its active region to produce a circuit which will amplify any small AC signal applied to its Base terminal with the Emitter grounded.

If a suitable DC “biasing” voltage is firstly applied to the transistors Base terminal thus allowing it to always operate within its linear active region, an inverting amplifier circuit called a single stage common emitter amplifier is produced.

One such *Common Emitter Amplifier* configuration of an NPN transistor is called a Class A Amplifier. A “Class A Amplifier” operation is one where the transistors Base terminal is biased in such a way as to forward bias the Base-emitter junction.


The result is that the transistor is always operating halfway between its cut-off and saturation regions, thereby allowing the transistor amplifier to accurately reproduce the positive and negative halves of any AC input signal superimposed upon this DC biasing voltage.

Without this “Bias Voltage” only one half of the input waveform would be amplified. This common emitter amplifier configuration using an NPN transistor has many applications but is commonly used in audio circuits such as pre-amplifier and power amplifier stages.


With reference to the common emitter configuration shown below, a family of curves known as the **Output Characteristics Curves**, relates the output collector current, (I_c) to the collector voltage, (V_{ce}) when different values of Base current, (I_b). Output characteristics curves are applied to the transistor for transistors with the same β value.

A DC “Load Line” can also be drawn onto the output characteristics curves to show all the possible operating points when different values of base current are applied. It is necessary to set the initial value of V_{ce} correctly to allow the output voltage to vary both up and down when amplifying AC input signals and this is called setting the operating point or Quiescent Point, **Q-point** for short and this is shown below.

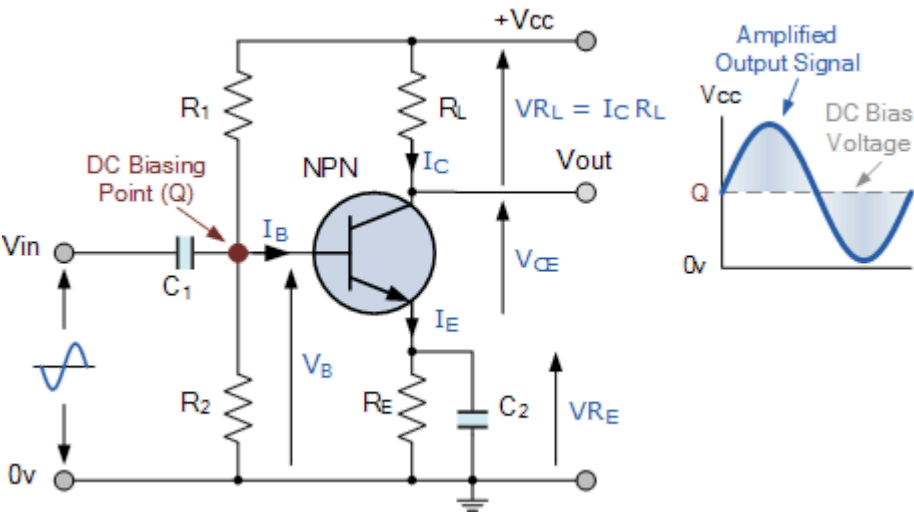Single Stage Common Emitter Amplifier Circuit



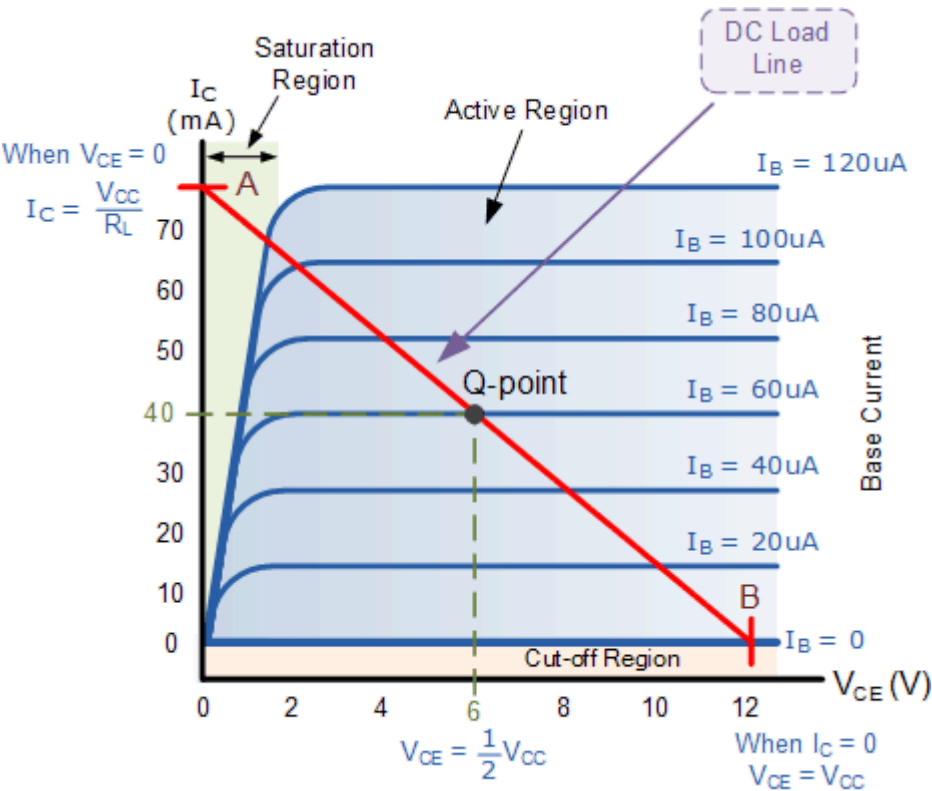Output Characteristics Curves of a Typical Bipolar Transistor



The most important factor to notice is the effect of V_{ce} upon the collector current I_c when V_{ce} is greater than about 1.0 volts. We can see that I_c is largely unaffected by changes in V_{ce} above this value and instead it is almost entirely controlled by the base current, I_b . When this happens we can say then that the output circuit represents that of a “Constant Current Source”.

It can also be seen from the common emitter circuit above that the emitter current I_e is the sum of the collector current, I_c and the base current, I_b , added together so we can also say that $I_e = I_c + I_b$ for the common emitter (CE) configuration.

By using the output characteristics curves in our example above and also Ohm’s Law, the current flowing through the load resistor, (R_L), is equal to the collector current, I_c entering the transistor which in turn corresponds to the supply voltage, (V_{CC}) minus the voltage drop between the collector and the emitter terminals, (V_{CE}) and is given as:

Collector Current, $I_C = \frac{V_{CC} - V_{CE}}{R_L}$

Also, a straight line representing the **Dynamic Load Line** of the transistor can be drawn directly onto the graph of curves above from the point of “Saturation” (A) when $V_{ce} = 0$ to the point of “Cut-off” (B) when $I_c = 0$ thus giving us the “Operating” or **Q-point** of the transistor. These two points are joined together by a straight line and any position along this straight line represents the “Active Region” of the transistor. The actual position of the load line on the characteristics curves can be calculated as follows:

When: ($V_{CE} = 0$) $I_C = \frac{V_{CC} - 0}{R_L}, I_C = \frac{V_{CC}}{R_L}$

When: ($I_C = 0$) $0 = \frac{V_{CC} - V_{CE}}{R_L}, V_{CC} = V_{CE}$

Then, the collector or output characteristics curves for **Common Emitter NPN Transistors** can be used to predict the Collector current, I_c , when given V_{ce} and the Base current, I_b . A Load Line can also be constructed onto the curves to determine a suitable Operating or **Q-point** which can be set by adjustment of the base current. The slope of this load line is equal to the reciprocal of the load resistance which is given as: $-1/R_L$

Then we can define a **NPN Transistor** as being normally “OFF” but a small input current and a small positive voltage at its Base (B) relative to its Emitter (E) will turn it “ON” allowing a much large Collector-Emitter current to flow. NPN transistors conduct when V_c is much greater than V_e .

In the next tutorial about **Bipolar Transistors**, we will look at the opposite or complementary form of the *NPN Transistor* called the PNP Transistor and show that the PNP Transistor has very similar characteristics to the bipolar NPN transistor except that the polarities (or biasing) of the current and voltage directions are reversed.

Read more Tutorials inTransistors

- [1. Bipolar Transistor](#)
 - [2. NPN Transistor](#)
 - [3. PNP Transistor](#)
 - [4. Transistor as a Switch](#)
 - [5. Junction Field Effect Transistor](#)
 - [6. The MOSFET](#)
 - [7. MOSFET as a Switch](#)
 - [8. Transistor Tutorial Summary](#)
 - [9. Darlington Transistors](#)
 - [10. FET Current Source](#)
 - [11. Open Collector Outputs](#)

215 Comments

Join the conversation

Error! Please fill all fields.

Your Name

Email Address

Write your comment here

☐ Notify me of follow-up comments by email.

Submit

• *Tusiime Godwin*

Good work

Posted on [June 28th 2022](#) | [7:44 am](#)

[Reply](#)

• *Sunday Adegunna*

If I_c is 0.12amps and the gain is 40. What will be the base current?
2 If I_c is 0.4 amps and the I_b is 0.002.amps, what will be the gain current.

Please, I need your help. And I wish to know more about transistor .

Posted on [June 20th 2022 | 4:31 am](#)
[Reply](#)

- Wayne Storr

1. As stated in the tutorial, $\beta = I_c/I_b$, thus: $I_b = I_c/\beta = 0.12/40 = 3\text{mA}$ or 0.003 amps
2. Again, $\beta = I_c/I_b = 0.4/0.002 = 200$.

Please make an effort to read the tutorial.

Posted on [June 20th 2022 | 7:17 am](#)
[Reply](#)

- Yohannes

Thanks a lot!
But I don't understand why you used two battery for one transistor. I mean can we not connect the collector terminal of the transistor to the base as +Vcc and the emitter of the transistor as 0V?

Posted on [May 28th 2022 | 9:00 pm](#)
[Reply](#)

- Wayne Storr

The tutorial shows, and explains, the biasing arrangements required for an NPN Bipolar Junction Transistor. Clearly, a single power supply would be used.

Posted on [May 30th 2022 | 7:48 am](#)
[Reply](#)

- Chaitanya Patange

My query is why Collector to emitter voltage should be same w.r.t original MPN while suggesting Alternate Part for existing MPN. Provide technical reason for that

Posted on [March 30th 2022 | 6:53 am](#)
[Reply](#)

- Mike Hartmann

EE495 course at URI. 1988 😊

Posted on [March 24th 2022 | 1:46 pm](#)
[Reply](#)

- Owen William Hanson

I'm trying to gather what the amplifiers that I see, with the power being (coming in on the emitter, the signal on the base and the amplifier (dual powered) outputs signal is taken off the collector), but every circuit description that I am reading discusses the circuit with the power coming in on the collector and the emitter is at the ground reference.

Posted on [February 24th 2022 | 11:19 pm](#)
[Reply](#)

- Marco

It's a didactical error to come up with this equation so late: $I_b = (V_b - V_{be}) / R_b$. It is fundamental for the entire story.

Posted on [February 24th 2022 | 6:16 pm](#)
[Reply](#)

- Atek Fr. Vince M

very helpful.....
it take long long to understand the transistors, but finally I got where to through.
As I was revising , everything was very easy and understandable

Posted on [January 07th 2022 | 8:43 pm](#)
[Reply](#)

- Sabra

Well and good

Posted on [December 14th 2021 | 7:58 pm](#)
[Reply](#)

- Inzam Haq

Good

Posted on [December 09th 2021 | 7:23 am](#)
[Reply](#)

- Alexandre

I'm very glad for this information

Posted on [September 16th 2021 | 7:23 pm](#)
[Reply](#)

- Godwin chikodi

Am Glad to get all this information here

Posted on [September 14th 2021 | 4:07 pm](#)
[Reply](#)

- Great

explain mor e on derivation of full wave rectifier

Posted on [July 20th 2021 | 12:24 pm](#)

[Reply](#)

- *Nii Bouncer* 🧑🏻 📌

R1=330k ,R3=1.3, hfe=150, vbe=0.6v, vcc=12v
Calculate Ib
Calculate Vcc

Posted on [July 07th 2021 | 11:47 am](#)
[Reply](#)

- *John Pless*

I wish there was more discussion about Re and C2. I’m guessing that there are some temperature effects which are being compensated for (?). I really want to know about these two components as we see them frequently but never explained.

Posted on [May 24th 2021 | 12:57 am](#)
[Reply](#)

- More

- *Raj kumar gotal*

Dhandar nots, excellent

Posted on [May 17th 2021 | 11:29 am](#)
[Reply](#)

- *Arief*

Mohon bantuan mengenai transistor vc089

Posted on [May 06th 2021 | 5:33 pm](#)
[Reply](#)

- *Isheanesu Makhuza*

How would you combine NPN and PNP transistors with an Op-amp to allow positive and negative current through the load?

Posted on [April 27th 2021 | 9:44 am](#)
[Reply](#)

- *Venkatabadarinath AYENAVOLU*

Intrasted

Posted on [April 23rd 2021 | 4:38 am](#)
[Reply](#)

- *Wainkem Destiny*

Will love to have a class

Posted on [April 20th 2021 | 3:26 pm](#)
[Reply](#)

